

Circuits Review

1. What is meant by a complete circuit?
A conducting Path From The "+" to the "-" Terminal
of a Battery (or Power supply)

2. Find the missing quantities in each of the following:

a) Potential difference is 120 V and the current is 25 A, what is the resistance?

$$R = \frac{V}{I} = \frac{120}{25} =$$

b) $R = 30 \Omega$ and the battery supplies 1.5 V, What is the current?

$$I = \frac{V}{R} = \frac{1.5}{30} =$$

c) If a 6 A current flows through a circuit with 100Ω resistance, what is the potential difference across the circuit?

$$V = I \cdot R = 6(100) = 600 \text{ Volts}$$

3. a) Would you be hurt if you fell from a building but arrested you fall by catching hold of just one high voltage power line? Explain your answer.

No There is No Potential difference along 1 power line

b) Would it make a difference if the line sagged until your feet touched the ground? Explain your answer.

YES, ONCE grounded you have ΔV

X Is the current from the outlets in your home AC or DC? AC

X ~~X~~ In the circuits in your home who supplies the electrons that vibrate in your wires, you or the power company?

~~X~~ Who supplies the energy that sets the electrons vibrating?

6. a) What type of current is supplied by batteries such as those found in your car or a DC. flashlight?

b) What are some possible sources of voltage? Power Supply, Battery, Solar

c) What causes charges to move through a conductor?

Potential difference

d) What are the appropriate units for voltage, current, resistance and power?

V \rightarrow Volts (V)

I \rightarrow Amps (A)

R \rightarrow ohms (Ω)

P \rightarrow Watts (W)

Electric Circuits

Physics First Honors 2010/11

7. Find the missing quantities in each of the following:

a) What would the current be through a 102 W bulb that operated on a 120 v source?

$$I = \frac{P}{V}$$
$$\frac{102}{120} = 0.85 \text{ A}$$

b) What is the power rating for a television that operates on 120 V at 5A?

$$P = IV = 120(5) = 600 \text{ W}$$

c) What is the voltage across a 70 W light bulb that has a current of 2 A?

$$V = P/I = 70/2 = 35 \text{ Volts}$$

8. What are the rules for a series circuit?

9. What are the rules for a parallel circuit?

11. Are the appliances in you home wired in parallel or series? How do you know?

Parallel, One turns off all the others stay on
They all operate @ 120 Volts

12. Why are fuses usually placed in a series between the power supply and a parallel circuit?

To protect the circuit from overloads

13. For the following questions assume all the resistors have the same resistance

In the following circuits:

a) Which bulb in each circuit would have the most current?

b) Which circuit has the largest total resistance? **A**

c) Which circuit has the largest total current? **C**

