
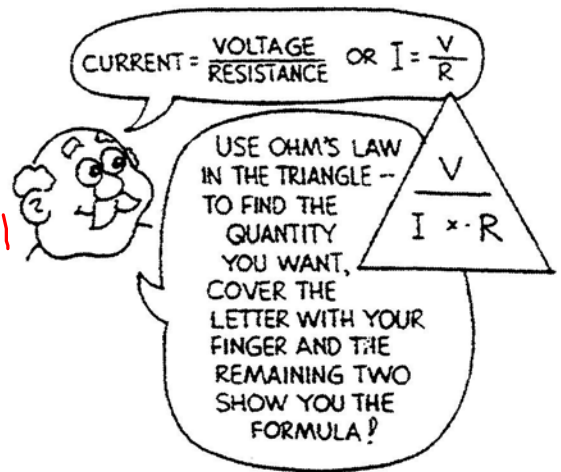


# Intro to OHM'S LAW

1. From the Ohm's Law lab, what relationship did you find between Current and resistance?

$IR = \text{CONSTANT}$   
 $I$  is Inversely Proportional to  $R$

2. Graph the relationship below:

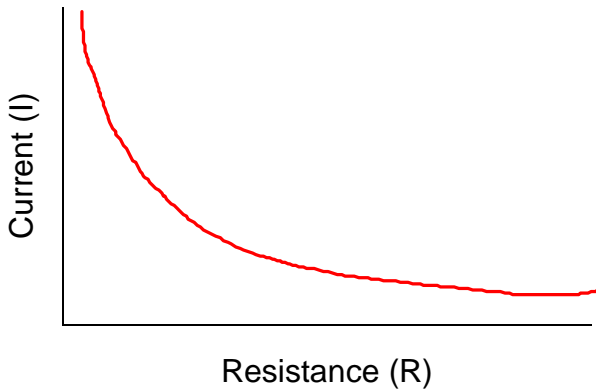

3. What is the equation for this relationship?

$I = \frac{\text{CONSTANT}}{R} \Rightarrow I = \frac{V}{R} \text{ or } V = IR$

4. How is Ohm's Law in electric circuits similar to Newton's Second Law in Mechanics?


$I = \frac{V}{R}$

$a = \frac{F}{m}$

- 1) Voltage causes current (Flow of  $e^-$ )
- 2) Resistance Reduces current (Flow of  $e^-$ )

- 1) FORCE Causes acceleration
- 2) mass (Inertia) Resists acceleration

## Intro to OHM'S LAW Example Problems

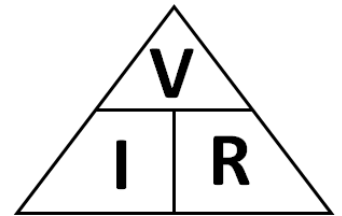

1. How much current flows in a 1000-ohm resistor when a voltage of 1.5 V is impressed across it?

$$I = \frac{V}{R} = \frac{1.5}{1000} = 1.5 \times 10^{-3} \text{ Amps} \\ 0.0015 \text{ Amps}$$

2. If the filament resistance in an automobile headlamp is 3 ohms, how much current does it draw when connected to a 12-V battery?

$$I = \frac{V}{R} = \frac{12}{3} = 4.0 \text{ Amps}$$

- b. What is the power rating of the bulb?

$$P = IV = (4.0)(12) = 48 \text{ watts}$$

3. What is the current in the 30-ohm heating coil of a coffee maker that operates on a 120-V circuit?

$$I = \frac{V}{R} = \frac{120}{30} = 4.0 \text{ Amps}$$



4. How much resistance allows an impressed voltage of 6 V to produce a current of 0.006 A?

$$V = IR \\ R = \frac{V}{I} = \frac{6}{.006} = 1000 \Omega$$

5. What is the voltage across a 100-ohm circuit element that draws a current of 1 A?

$$V = IR = (1)(100) = 100 \text{ Volts}$$

6. The current in an incandescent lamp is 0.5 A when the lamp is connected to a 120-V circuit, and 0.2 A when it is connected to a 10-V source. Does the resistance of the lamp change in these cases? Explain your answer and defend it with numerical values.

$$(120) \quad R = \frac{V}{I} = \frac{120}{0.5} = 240 \Omega \quad \text{Brighter} \checkmark$$

$$(10) \quad R = \frac{V}{I} = \frac{10}{.2} = 50 \Omega$$

Brighter = Hotter = Hotter = R ↑

**Ohm's Law - Problem set 1**

**$V = I \cdot R$**

**$P = I \cdot V$**

**$Energy\ converted = Power \times Time$**

1. Find the missing quantities in each of the following:
  - a) Potential difference is 120 V and the current is 30 A, what is the resistance? (4  $\Omega$ )
  
  - b)  $R = 30\Omega$  and the battery supplies 5.0 V, What it the current? (0.167 A)
  
  - c) If a 6 A current flows through a circuit with 200  $\Omega$  of resistance, what is the potential difference across the circuit? (1200 V)
  
2. An electric heater produces heat by applying a potential difference of 50 V across a nichrome wire with a total resistance of 8.0 $\Omega$ .
  - a) find the current in the wire (6.25 A)
  
  
  - b) Determine the power rating of the heater. (313 W)
  
3. A potential difference or 120 V is applied across a 75 W light bulb.
  - a) Find the current flowing through the bulb (0.63 A)
  
  
  - b) Determine the resistance of the bulb. (190 $\Omega$ )
  
4. How much does it cost to burn a 100 W bulb for 24 hours if electricity cost \$0.08 per kilowatt-hour? (Remember that a kilowatt-hour is a unit of energy) - USE THE FACTOR LABEL METHOD, KEEP TRACK OF UNITS (\$0.19)